

Instrumentation Development for a 5 GHz Receiver for a Radioastronomy Experiment

Miguel Bergano

Luis Cupido, Domingos Barbosa, Rui Fonseca, George Smoot


Overview

- ◆ The meaning of CMBR;
- ◆ Description of a Galactic Experiment Project;
- ◆ Types of radiometer
- ◆ Description of the Superheterodyne Receiver of GEM;
- ◆ Development of a Very Low Noise Amplifier for this Project (applicable to other RA projects)
- ◆ Full Digital Back-end;


What is CMBR?




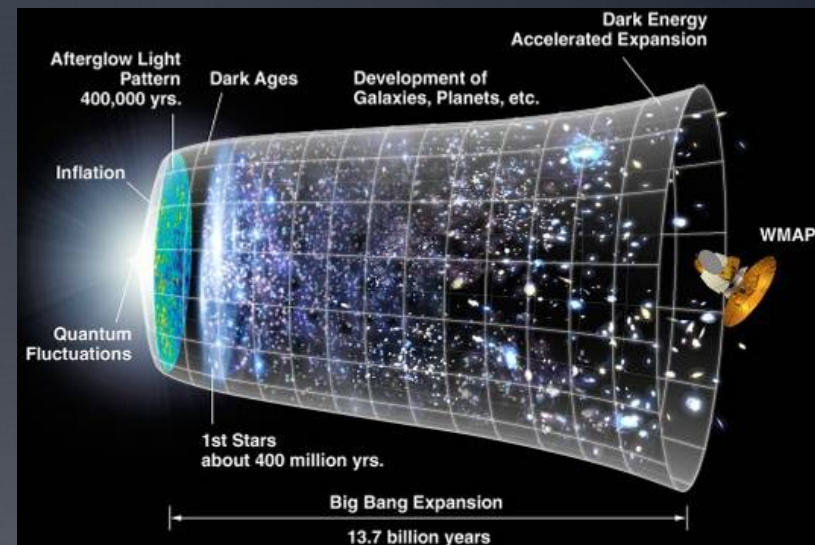
- ◆ Cosmic Microwave Background Radiation
- ◆ Best “Big-Bang” relic (Fossil);
- ◆ First Sky map: 1992 by COBE satellite COBE (PI G. Smoot, was awarded the Physics Nobel Prize in 2006 for this discovery)
- ◆ CMBR fluctuations (anisotropies) allow to determine the geometry, age of the Universe.




CMBR

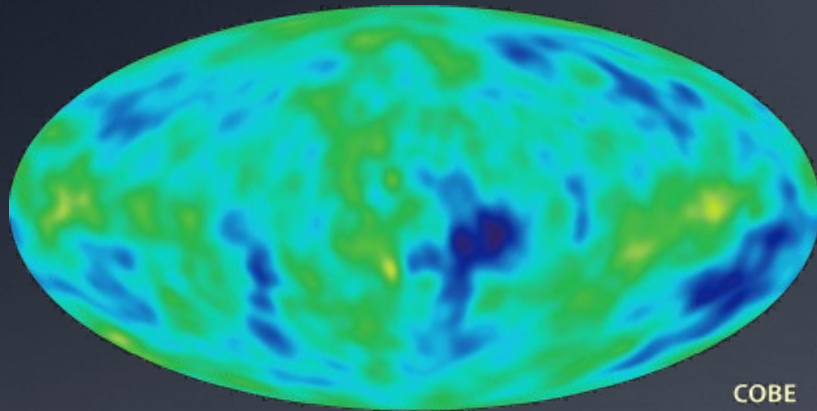

COBE

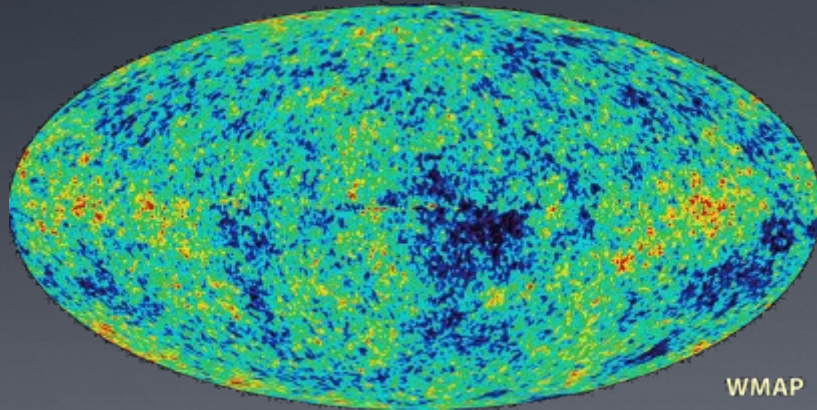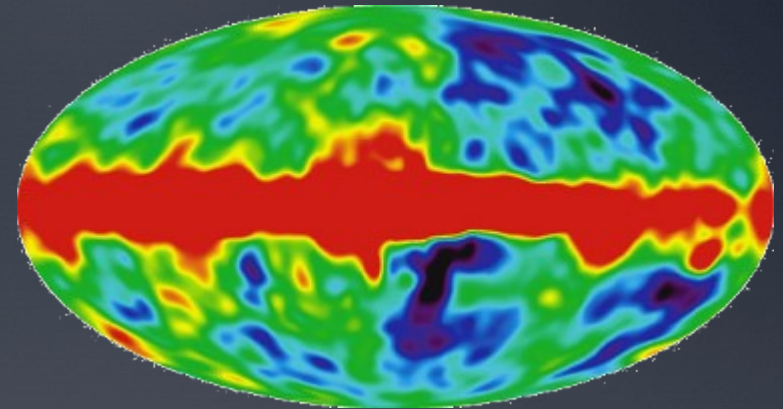

WMAP


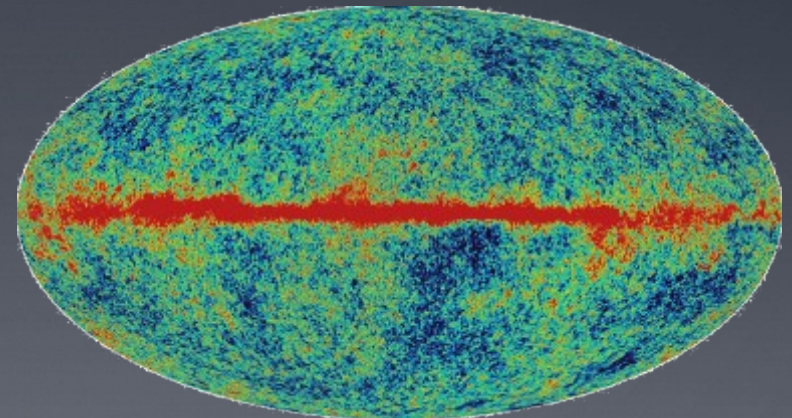


Maps provided by NASA/WMAP

**GEM : auxiliar experience to
Planck Surveyour (ESA 2009)**





GEM – Galactic Emission Mapping

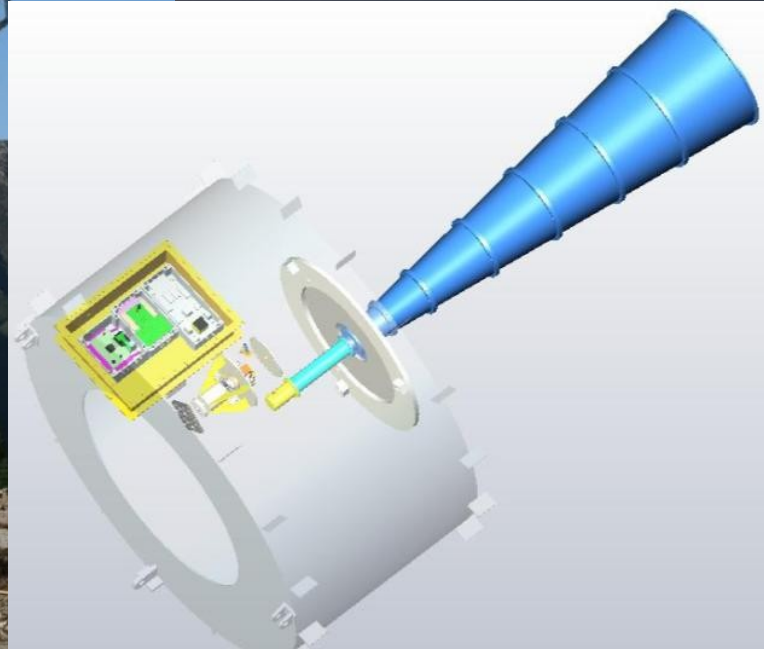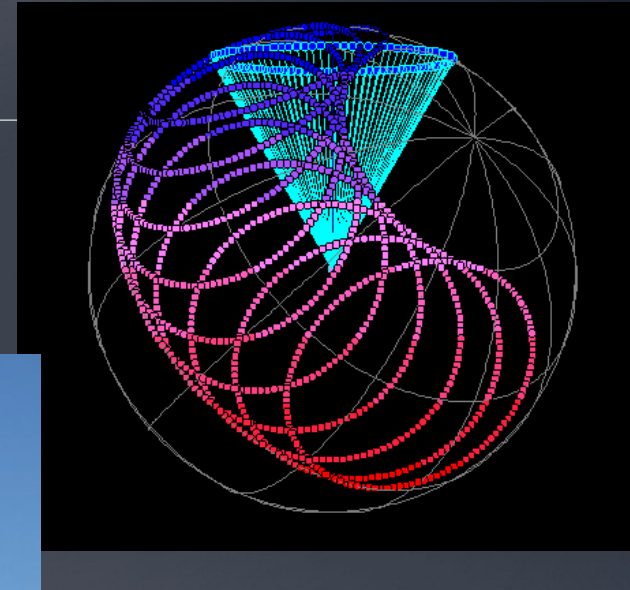- ◆ North/South Hemisphere (Portugal and Brasil)
- ◆ 80% sky coverage




5 GHz Portugal and Brazil Surveys

Coverage simulations

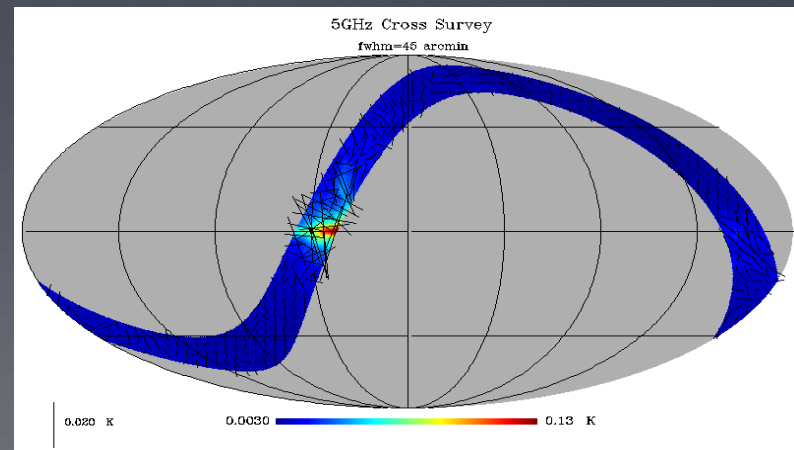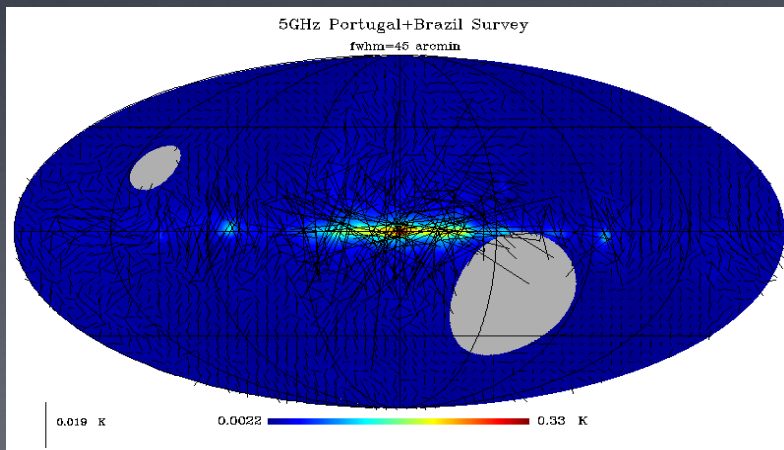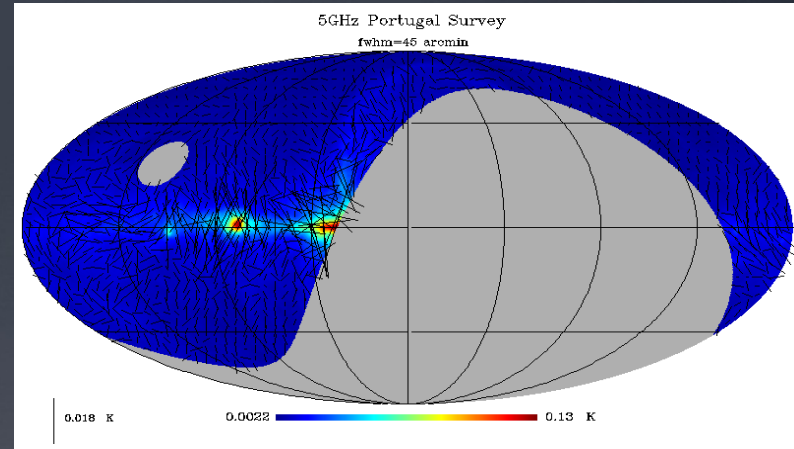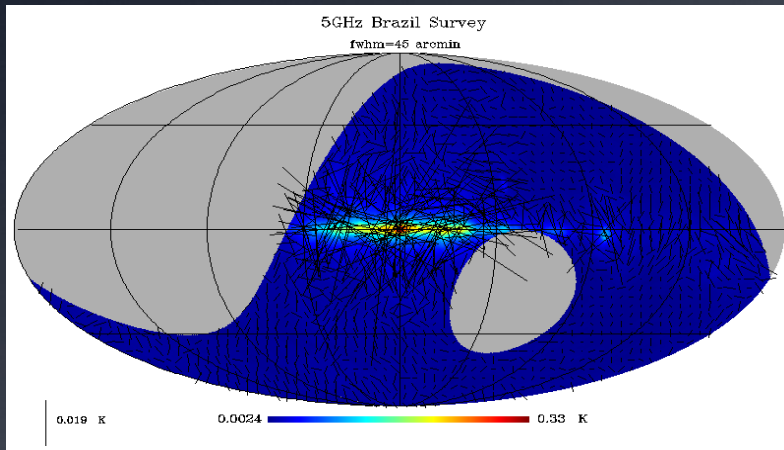


Radiometer?

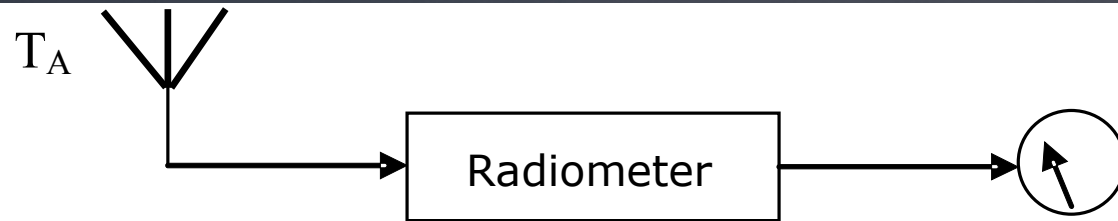- ◆ High sensitivity, well calibrated microwave receiver;
- ◆ Detect and measure celestial sources;



$$P = KBGT_A \text{ Watts,}$$
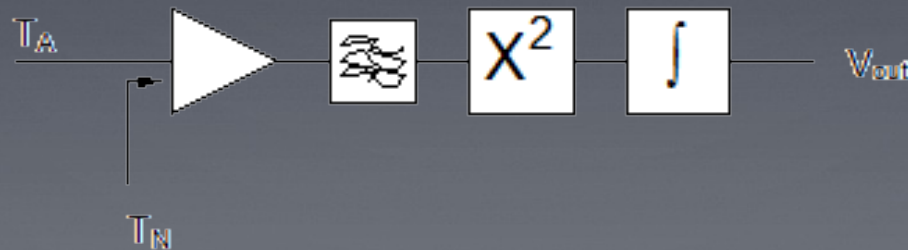
$$K - \text{ Boltzmann Constant } = 1,38 \times 10^{-23} \text{ J/K}$$




Radiometer Types

Amplification:

- ◆ Direct;
- ◆ Superheterodyne


Accuracy:

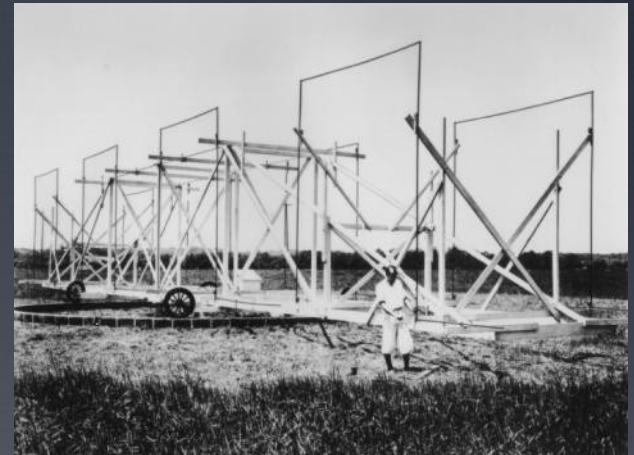- ◆ Dicke Radiometer
- ◆ Noise Injection Radiometer
- ◆ Total Power Radiometer




$$\Delta T = 2 \cdot \frac{T_A + T_N}{\sqrt{B \cdot \tau}}$$

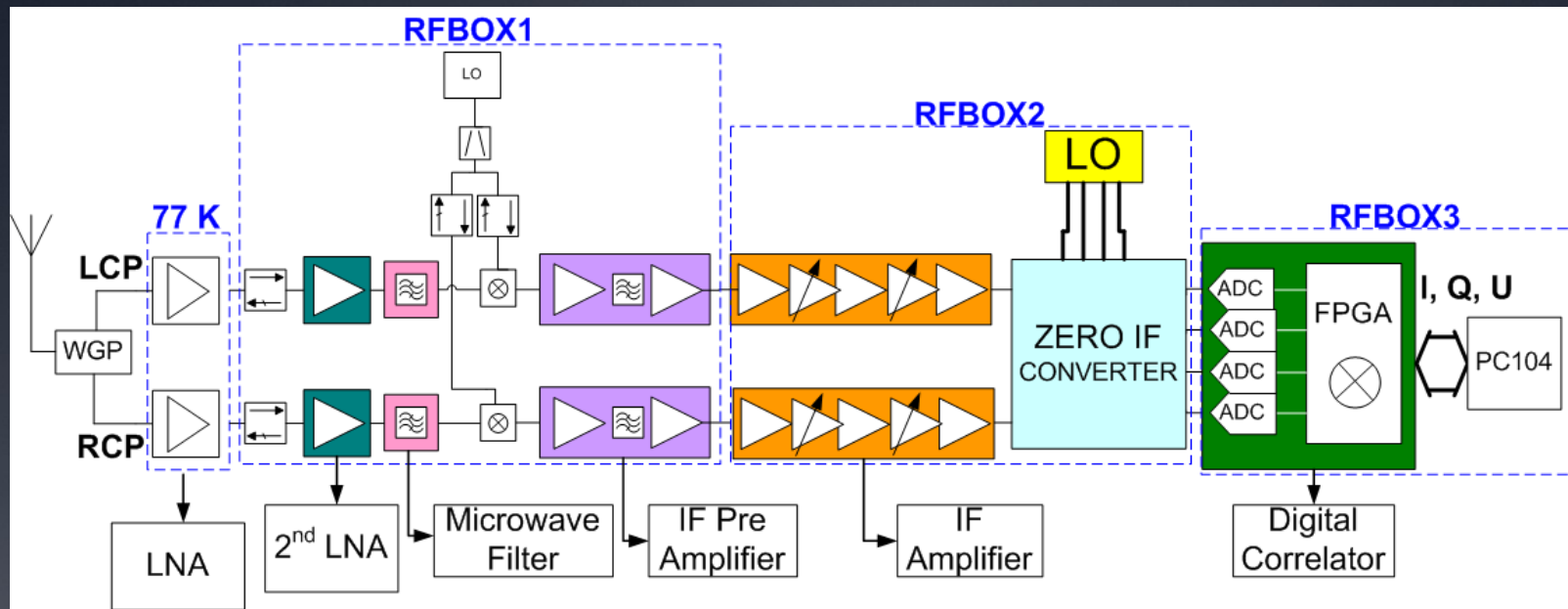Superheterodyne Receiver (Base-band Complex Correlator)



Novel approach to digital correlators

Receiver

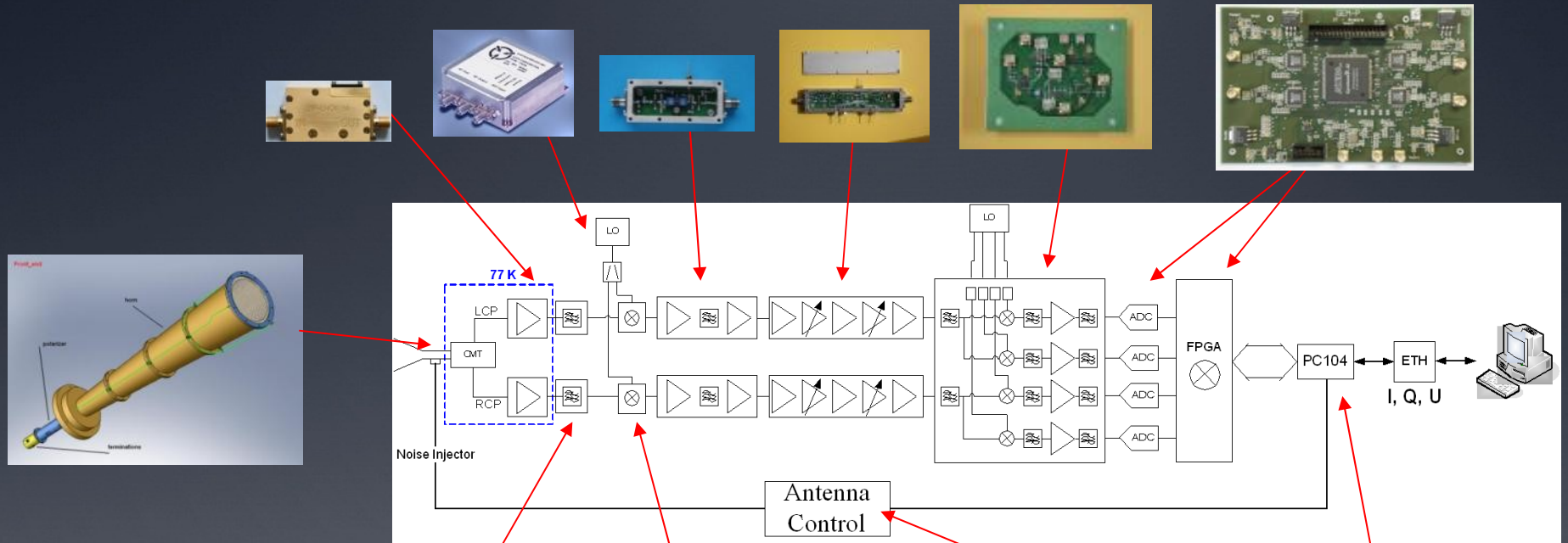

Gain_{TOTAL} = 104 dB

F_{TOTAL} = 6,1K

Receiver Characteristics

- **System Temperature about ~ 20K**
- **Sensitivity ~ $2\text{mKs}^{-1/2}$**
- **Frequency 5GHz with 200MHz Bandwidth**
- **Gain ~ 100dB**
- **Suitable for Stokes Parameters Calculation**
- **LNA Cryocooled pHEMT Amplifiers**

2° LNA Requirements

- **Working at environment Temperature.**
- **Frequency 5GHz**
- **Gain ~ 13dB**
- **GaAs pHEMT or HJFET Amplifiers**
- **Noise Figure below 0,65 dB**
- **Main function is to reduce the noise contribution of the RF passive Filter and Mixer.**

NF contribution

- Introducing a LNA between the cryogenic one and the set filter, mixer and pre-amplifier reduces the contribution of the later devices

	LNA	2 nd LNA	Filter + Mixer + IF Pre Amplifier
T _{eq}	6K	36K	6202K
NF	0,3dB	0,5 dB	13,5 dB
Gain	36 dB	13 dB	20 dB
Linear Gain	3891	20	100

$$F = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2}$$


$$F_{2^{nd}LNA} = 6,08$$

$$F_{without\ 2^{nd}LNA} = 7,59$$

First Approach


- The development of an amplifier starts by defining two main characteristics:
 - Maximum Gain – more current
 - Minimum Noise – less current

$$G = \frac{1 - |G_s|^2}{|1 - S_{11}G_s|^2} |S_{21}|^2 \frac{1 - |G_L|^2}{|1 - S_{22}G_L|^2}$$

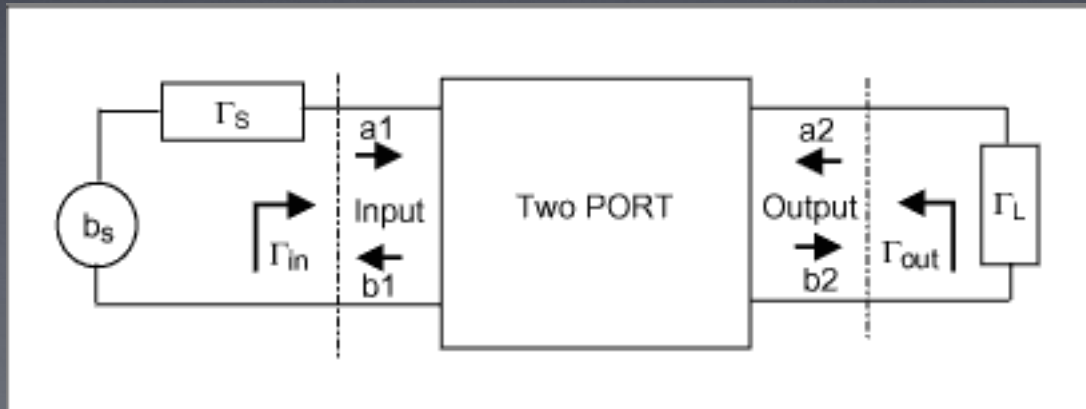


Statements

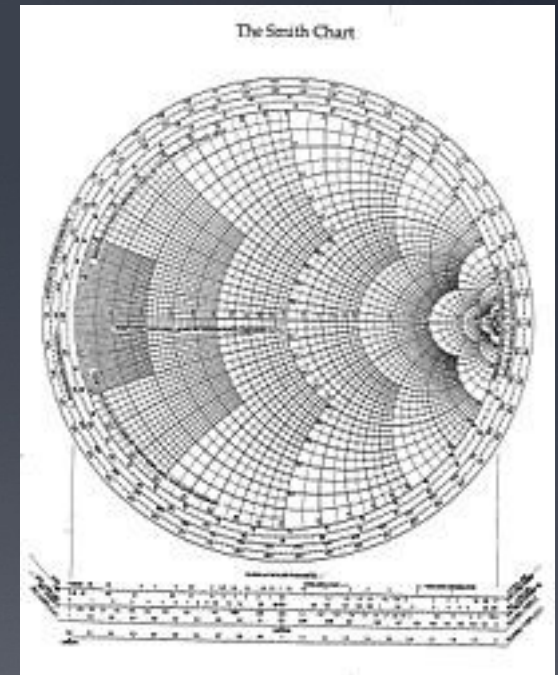- Γ_{OPT} , r_n and NF_{min} are the provided
- Noise Circles and Gain Circles are designed
- Selecting the best suitable impedances for G_L and G_S
- But it is an Unilateral device $S_{12} \neq 0$, so:
 - G_L or G_S must consider the influence on each one



Noise and Gain Compromise

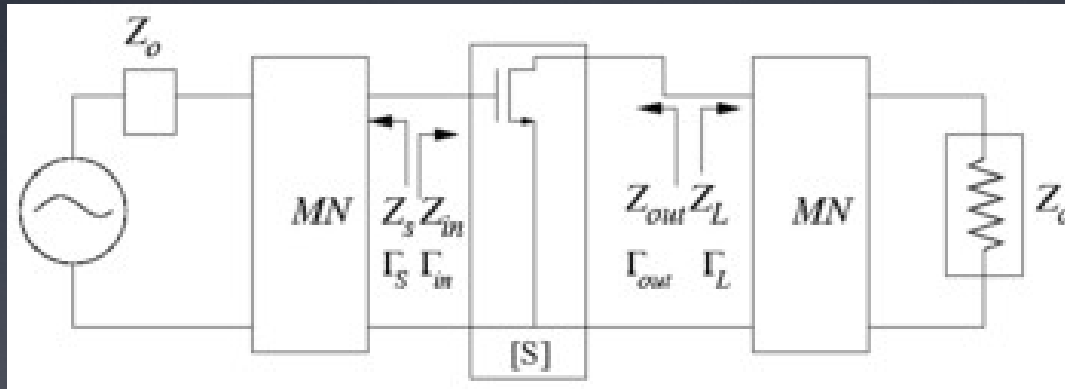- In order to obtain the best performance for noise G_s must be matched for Γ_{OPT}



- The bilateral case implies the output to be matched considering the input matching network

Commercial Availability

- GaAs pHEMT and HJFET Low Noise Transistors
- Noise Figure between 0,3 and 0,6 dB
- Total Gain approximately 12/13 dB
- Noise and S-parameters Provided by manufacturer
- Substrate to be used: RT5880 (low $\epsilon_r=2,2$)

	Company	NF (dB)	GAIN (dB)	@Freq. (GHz)
MGF4953	Mitsubishi	0,40	13,5	12
MGF4941	Mitsubishi	0,35	13,5	12
MGF4419	Mitsubishi	0,50	12	12
ATF-36077	Agilent	0,5	12	12
MGF4931	Mitsubishi	0,60	11,5	12
NE3511S02	NEC	0,30	13,5	12
FHX13X	Fujiitsu	0,45	13	12


ATF-36077 Typical Noise Parameters,

Common Source, $Z_0 = 50 \Omega$, $V_{DS} = 1.5 \text{ V}$, $I_D = 10 \text{ mA}$

Freq. GHz	$F_{min}^{[1]}$ dB	Γ_{opt}		R_n/Z_0 -
		Mag.	Ang.	
1	0.30	0.95	12	0.40
2	0.30	0.90	25	0.20
4	0.30	0.81	51	0.17
6	0.30	0.73	76	0.13
8	0.37	0.66	102	0.09
10	0.44	0.60	129	0.05
12	0.50	0.54	156	0.03
14	0.56	0.48	-174	0.02
16	0.61	0.43	-139	0.05
18	0.65	0.39	-100	0.09

Circles

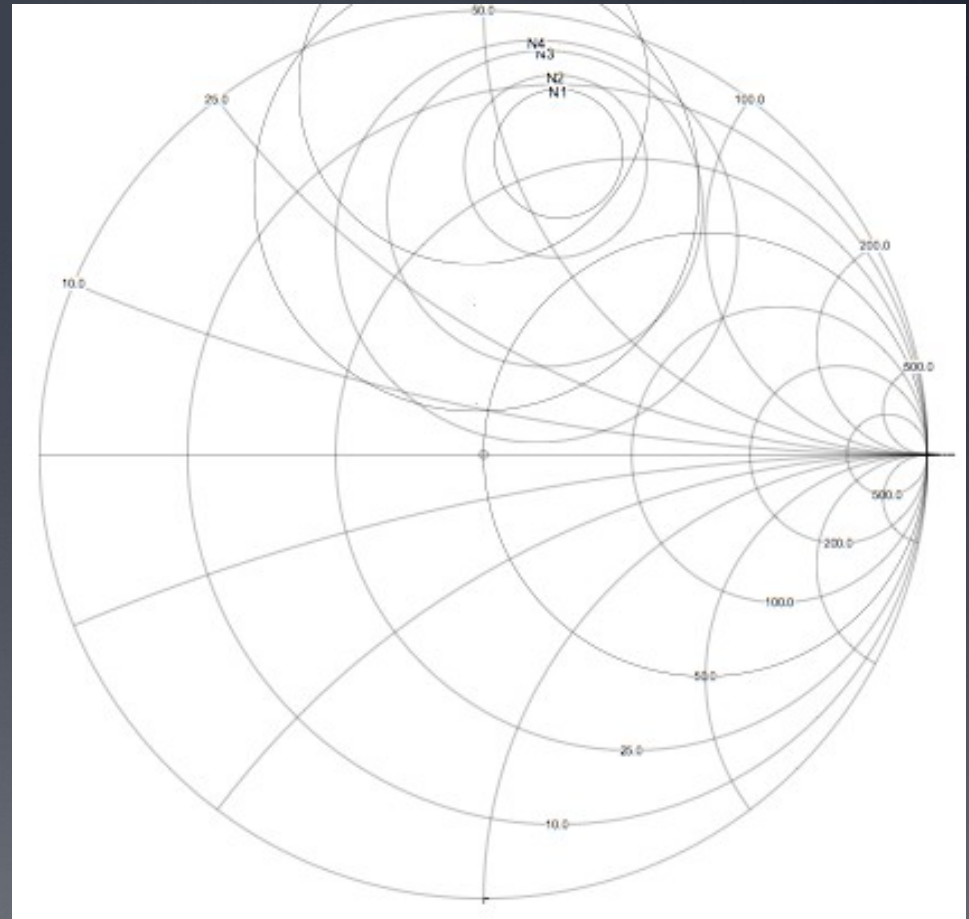
- Noise circles for ATF-36077
- $N_{fmin}=0,3\text{dB}$
 - $N_1=0,35\text{dB}$
 - $N_2=0,4\text{dB}$
 - $N_3=0,6\text{dB}$
 - $N_4=0,8\text{dB}$
- Maximum gain = $18,4\text{dB}$
 - $G_1=15\text{dB}$




Matching Networks

- Since the transistors are packaged (MMIC) the network should match 50 ohm to Γ_{OPT}
- Considering the previous network determine the new Z_{out}
- Match Z_{out} for 50 ohm

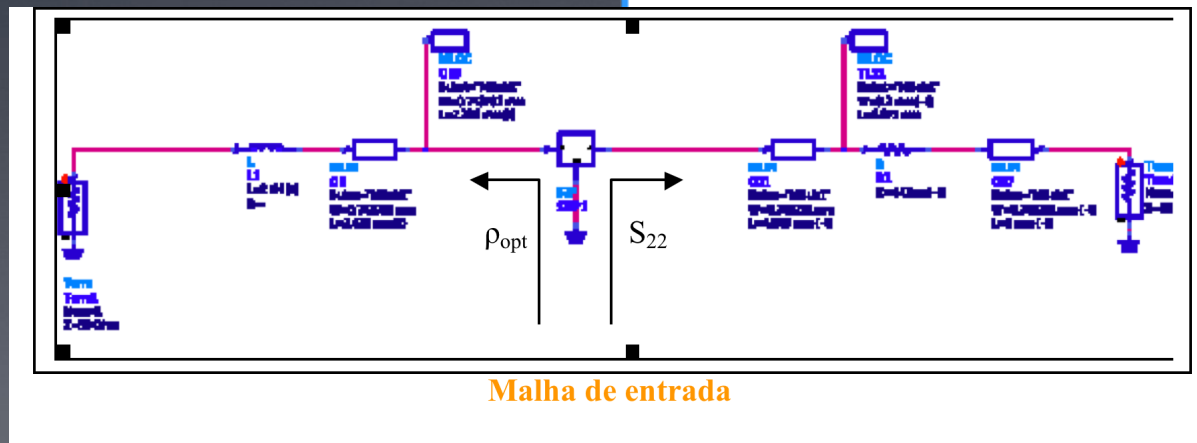
$$\Gamma_{OUT} = S_{22} + \frac{S_{12}S_{21}G_S}{1 - S_{11}G_S}$$



Input Matching Network

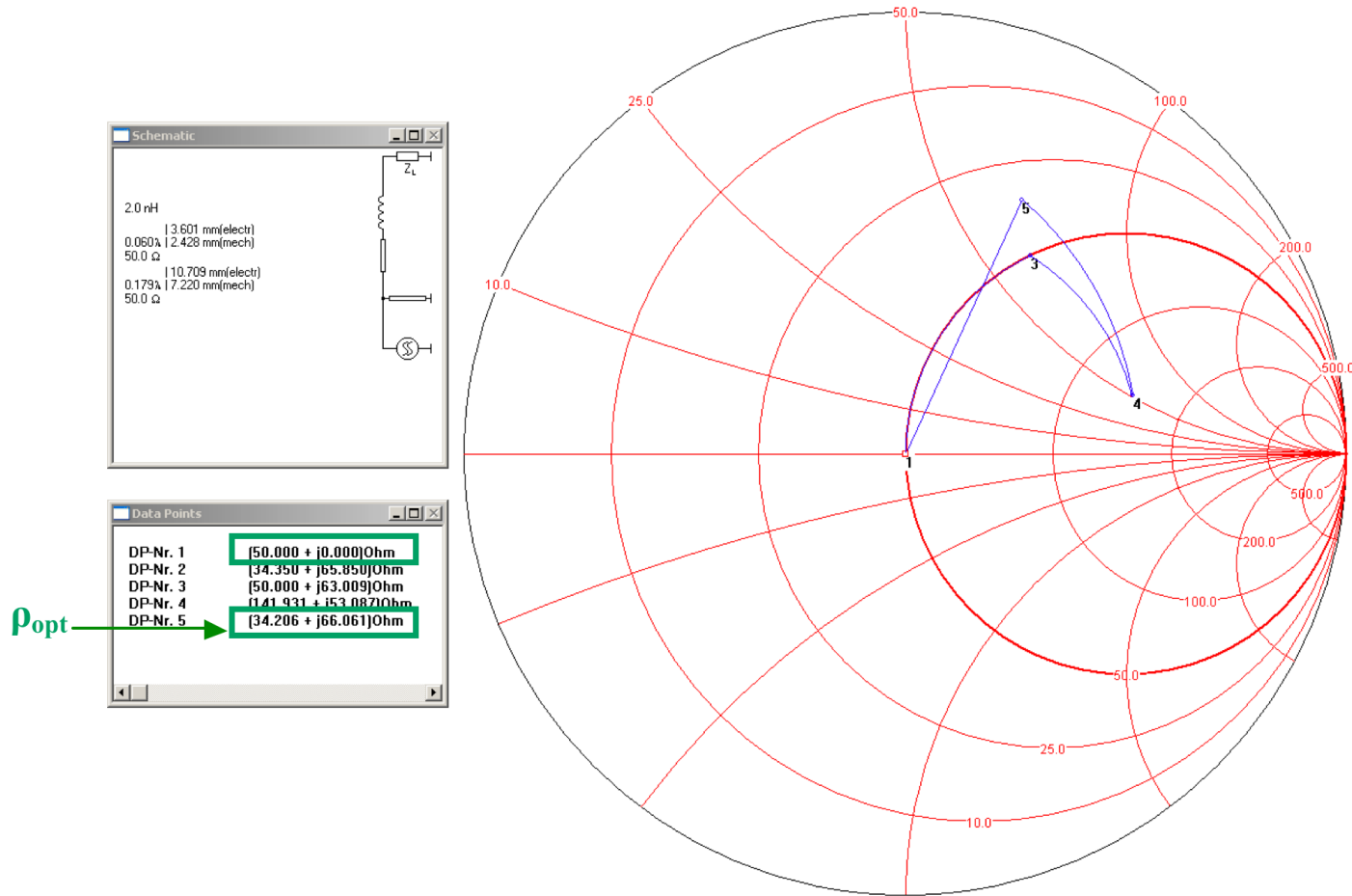

Output Matching Network

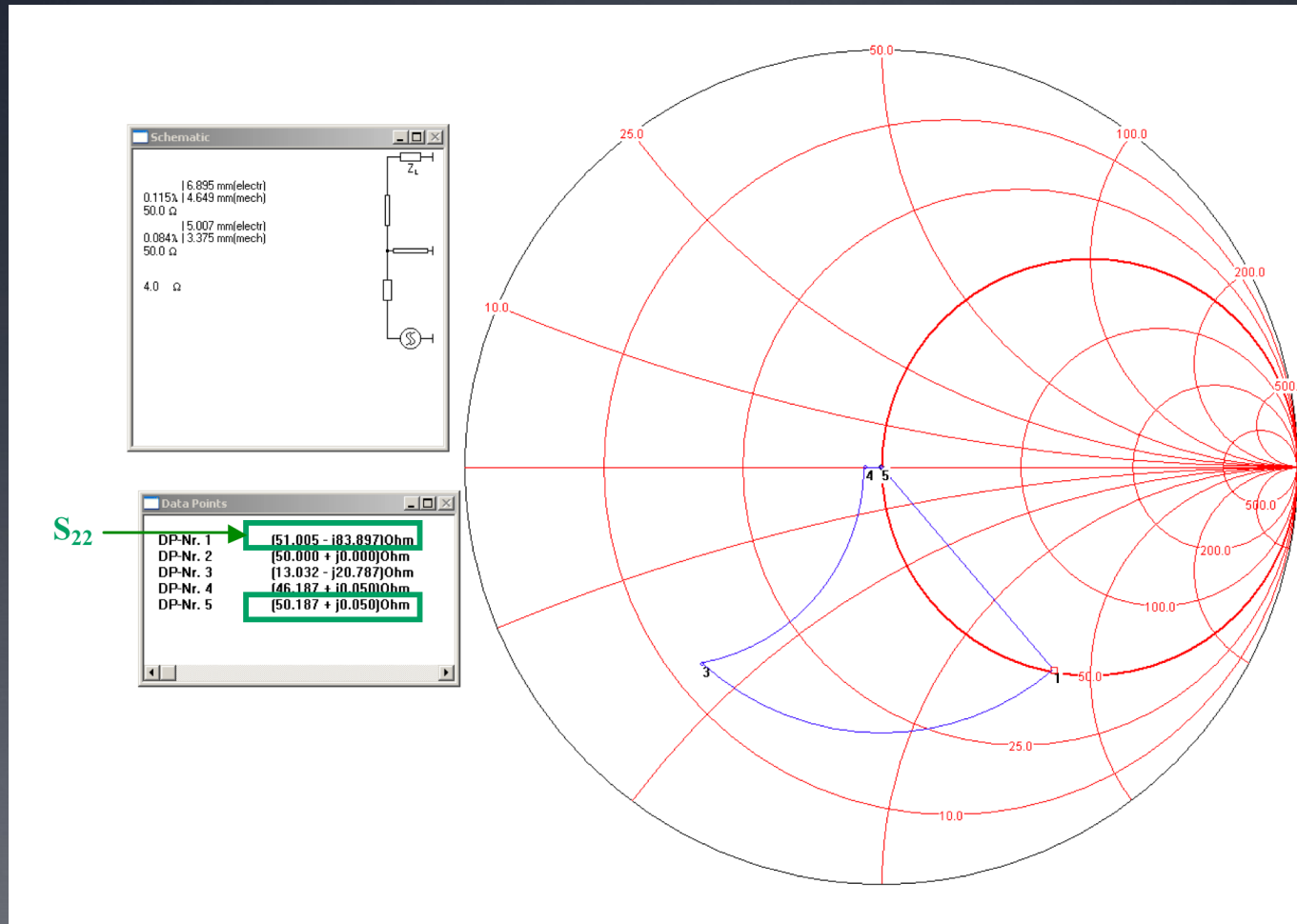

SIMULATIONS

- **S and Noise Parameters provided by the manufacturer**
- **Challenge is to create good matching networks, that will provide the lowest NF;**
- **Obtain low NF for a wide frequency band.**



Device	NF(dB @ 5GHz)	GAIN(dB @ 5GHz)
MGF4941 from Mitsubishi	0,25	13,8
MGFC4419 from Mitsubishi	0,28	12,3
MGF4931 from Mitsubishi	0,48	11
ATF-36077 from Agilent	0.38	13
NE3511S02 from NEC	0,25	13
FHX13X from Fujitsu	-----	14

- **The described procedure was applied for each device**

Design Constraints


Using the Noise Parameters provided, and following the usual procedure to design an input and output matching networks, a LNA with $NF=0,38$ dB and 13,4dB of gain was implemented

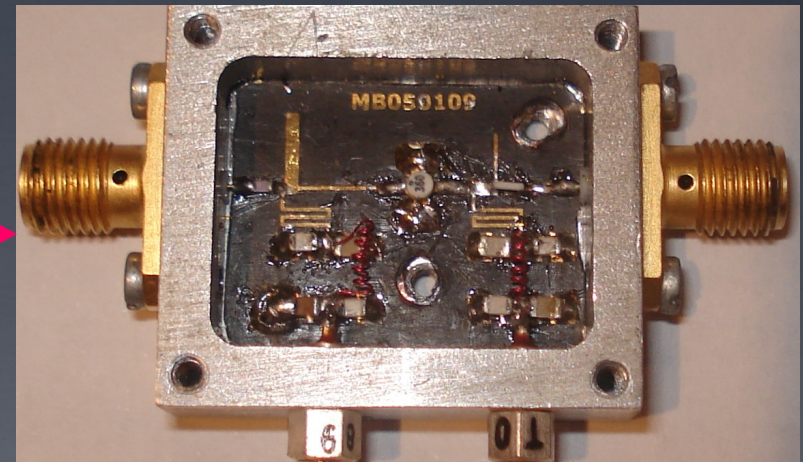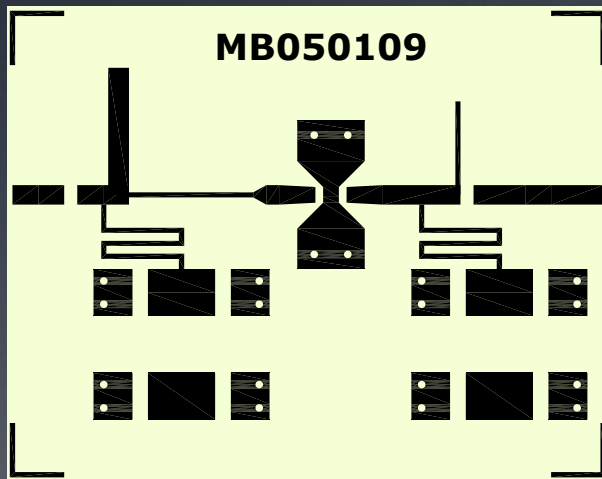Designed with the help of a vectorial tool, AUTOCAD




Avago ATF-36077 Results



Noise Figure

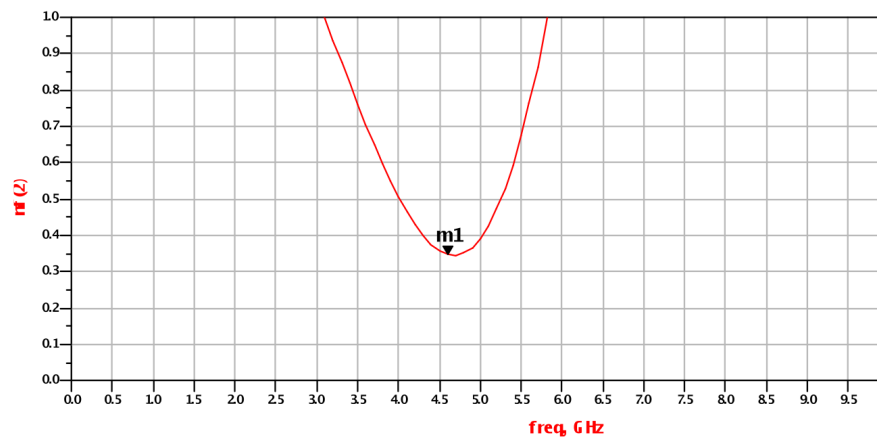

Gain

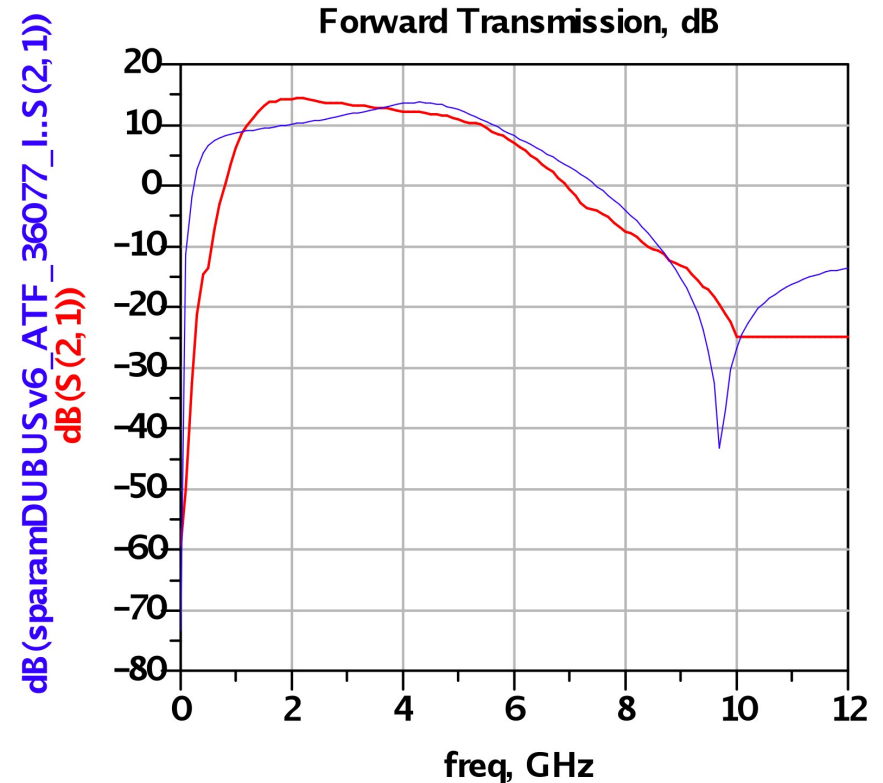

Noise Figure Measurements

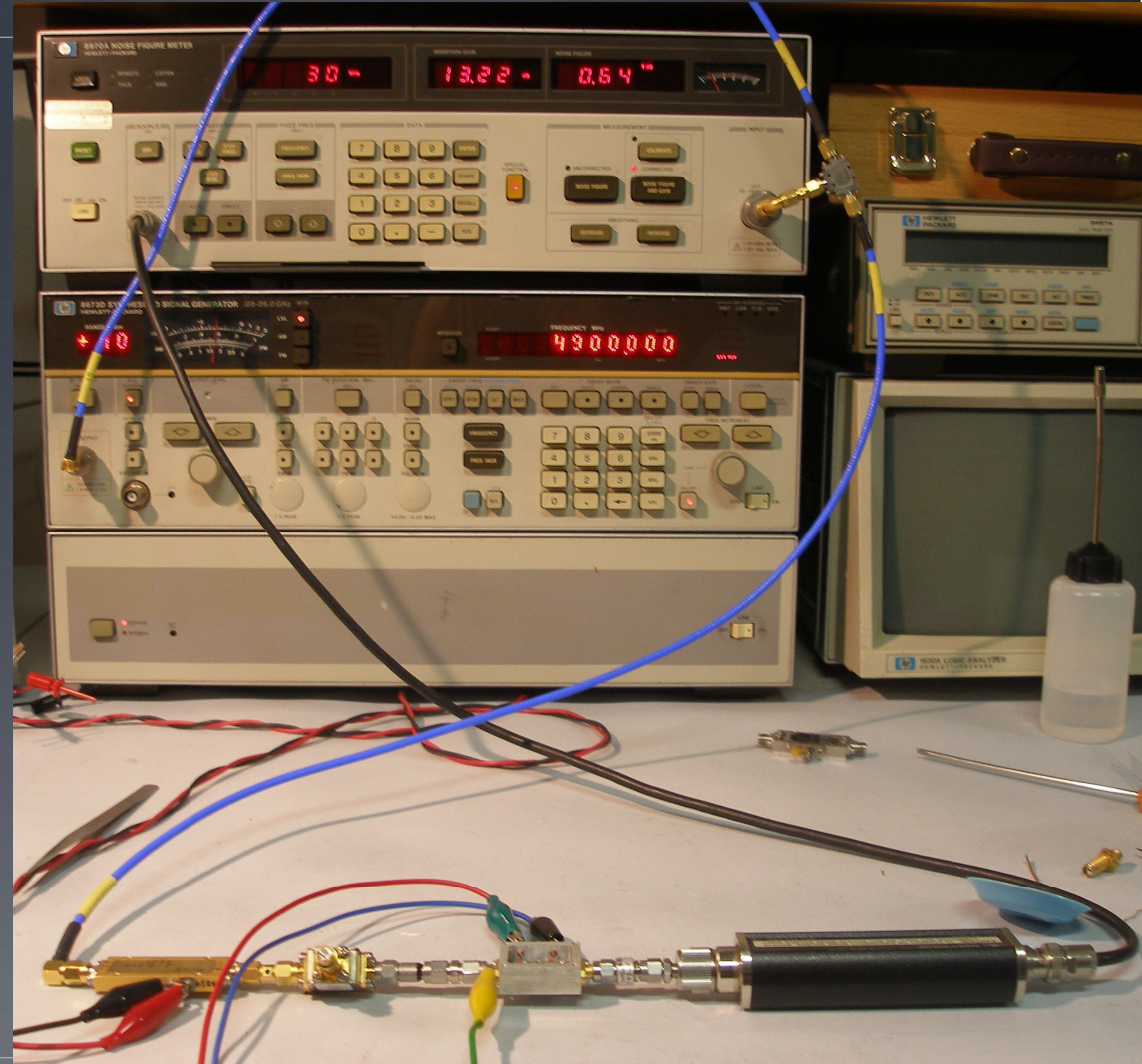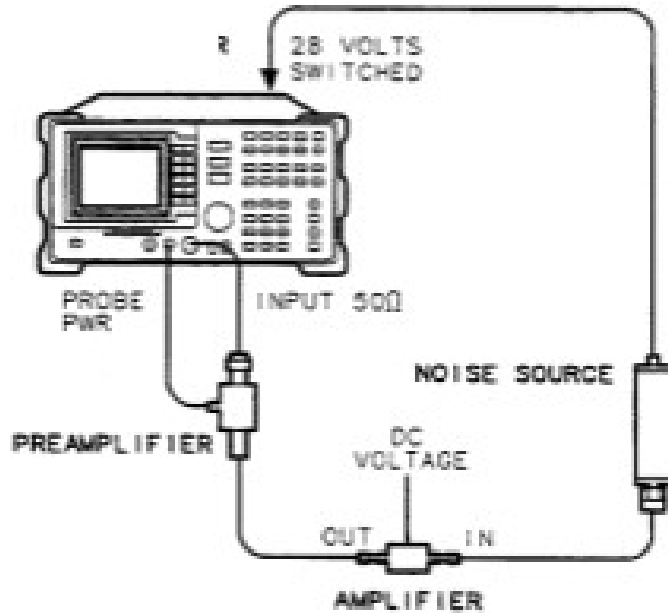

IF part designed and tested

B=200MHz; 31dB; Butterworth
MMIC (best response flatness)


4.9GHZ; B=600MHz
Coupled Line filter
RO4003



Flat gain; 71dB;
Digital attenuation



IF Chain+RF Filter

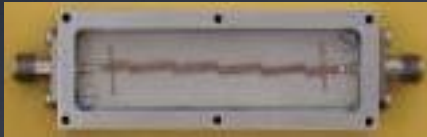


120dB isolation between ports



Frequency 600MHz; VCO; MMIC Amp.;
PLL synthesizer; 7dBm

Digital Correlator

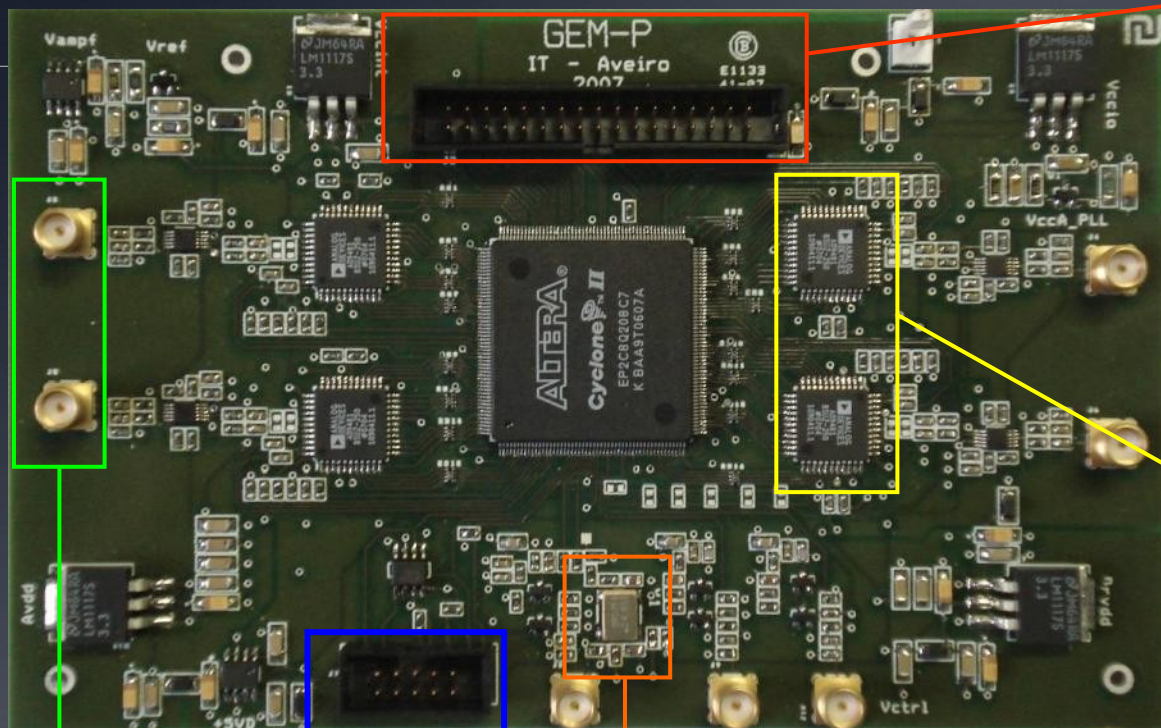

ISA Interface output

$$RL = \Re(E_{rcp} E_{lcp}^*) \rightarrow \text{Stokes } U$$

$$LR = \Re(E_{rcp, -\frac{\pi}{2}} E_{lcp}^*) \rightarrow \text{Stokes } Q$$

$$RR + LL = \langle E_{rcp} E_{rcp}^* \rangle + \langle E_{lcp} E_{lcp}^* \rangle \rightarrow \text{Stokes } I$$

- ADCs AD9481 from Analog Devices.
- 250 Msp/s
- 8 bits of resolution

Analog inputs

Active Serial mode programming interface

Crystal Oscillator 100 MHz

- **FPGA EP2C8Q208C7 Cyclone II from ALTERA**
- 8256 LE.
- Number of 9 bits multipliers = 36;
- 208 pins
- Speedgrade 7

Main Features of PC104 (MOPSIcdLX*)



* www.kontron.com/MOPS


◆ Hardware

- 500 MHz AMD LX800™ Processor
- 256 MByte DDR-RAM
- ChipDisk IDE 1 GByte
- Support: ISA, Ethernet
- Power supply: 5V


◆ Software

- Linux, kernel 2.4
- **Dedicated, custom-made software for FPGA communication via ISA bus (C lang. – implemented by Francisco Fernandes).**
- SSH File transfer.

Mechanical Layout

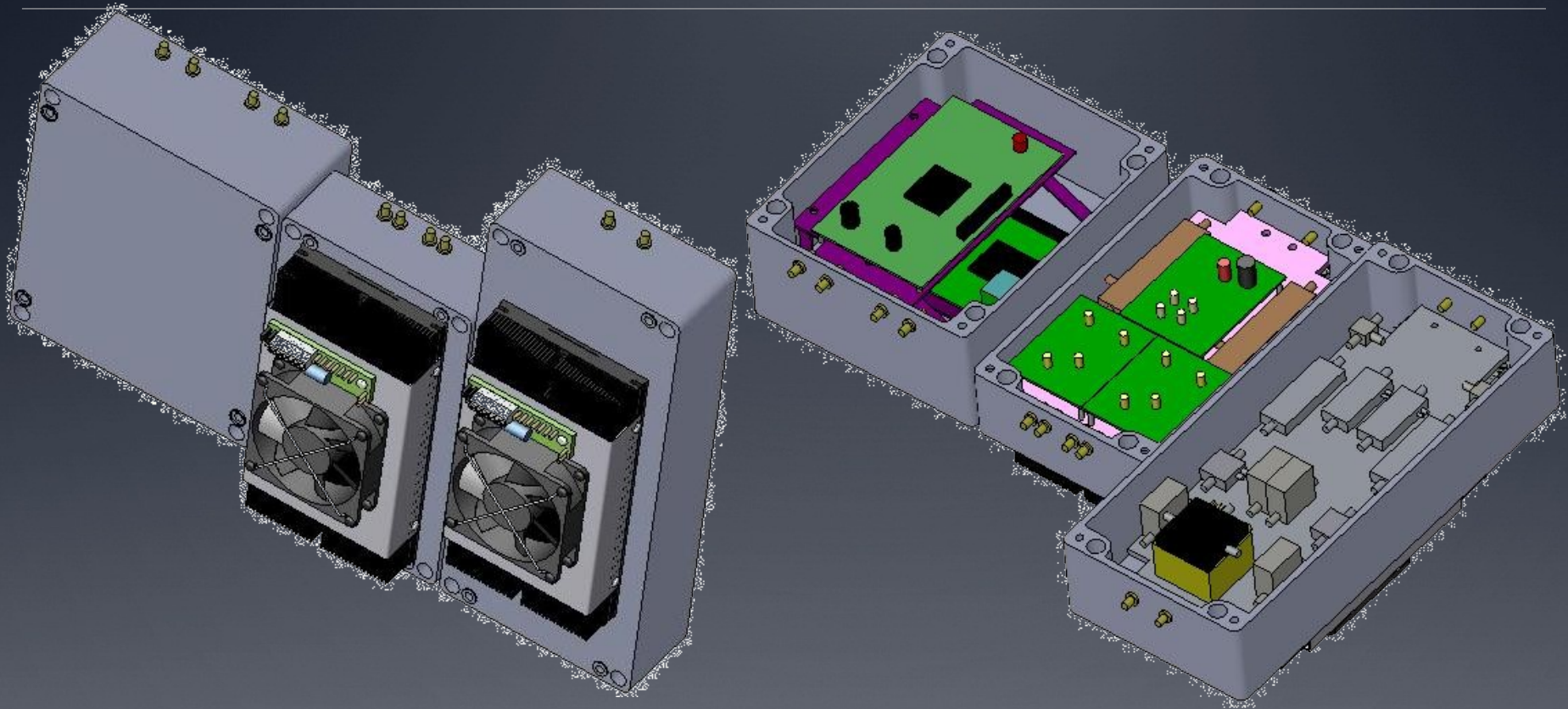


Receiver photo

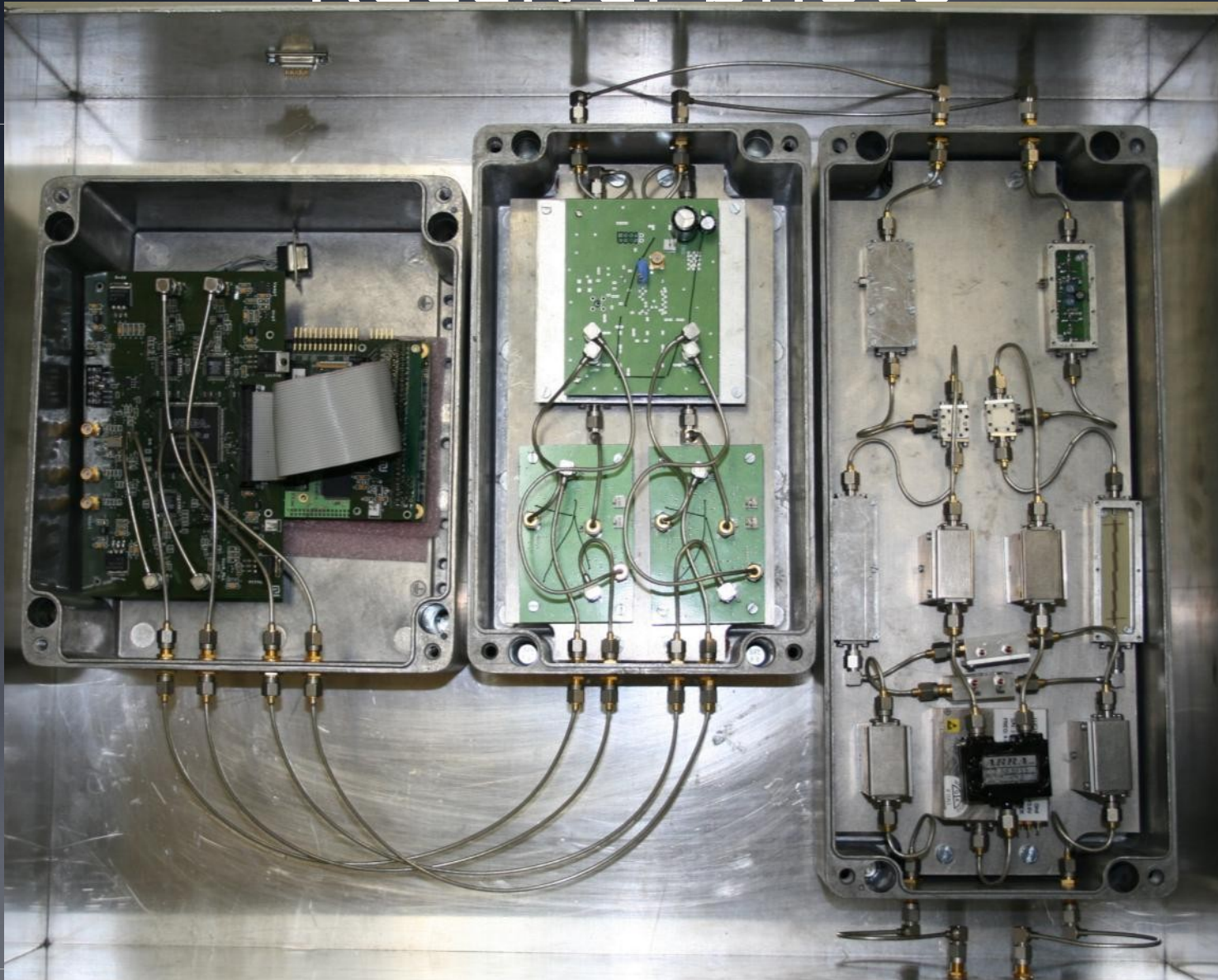

Conclusion : Radiometer facts


- $T_{\text{sys}} < 20 \text{ K}$; $B = 200 \text{ MHz}$; 104 dB gain
- High-performance IF strip
- Latest RF tech+ microstrip design + MMIC
- Zero-IF Converter + I,Q modulation
- Digital Correlator : 4-channel, FPGA implemented processing 16 Gbps !
- An SKA (Potential!) Digital Demodulator
- Dynamic Range: Total= 20 dB , Instantaneous= 80 dB
- Suitable for state of the art RA applications.
- MoU with ESA Planck Science Team.

Future

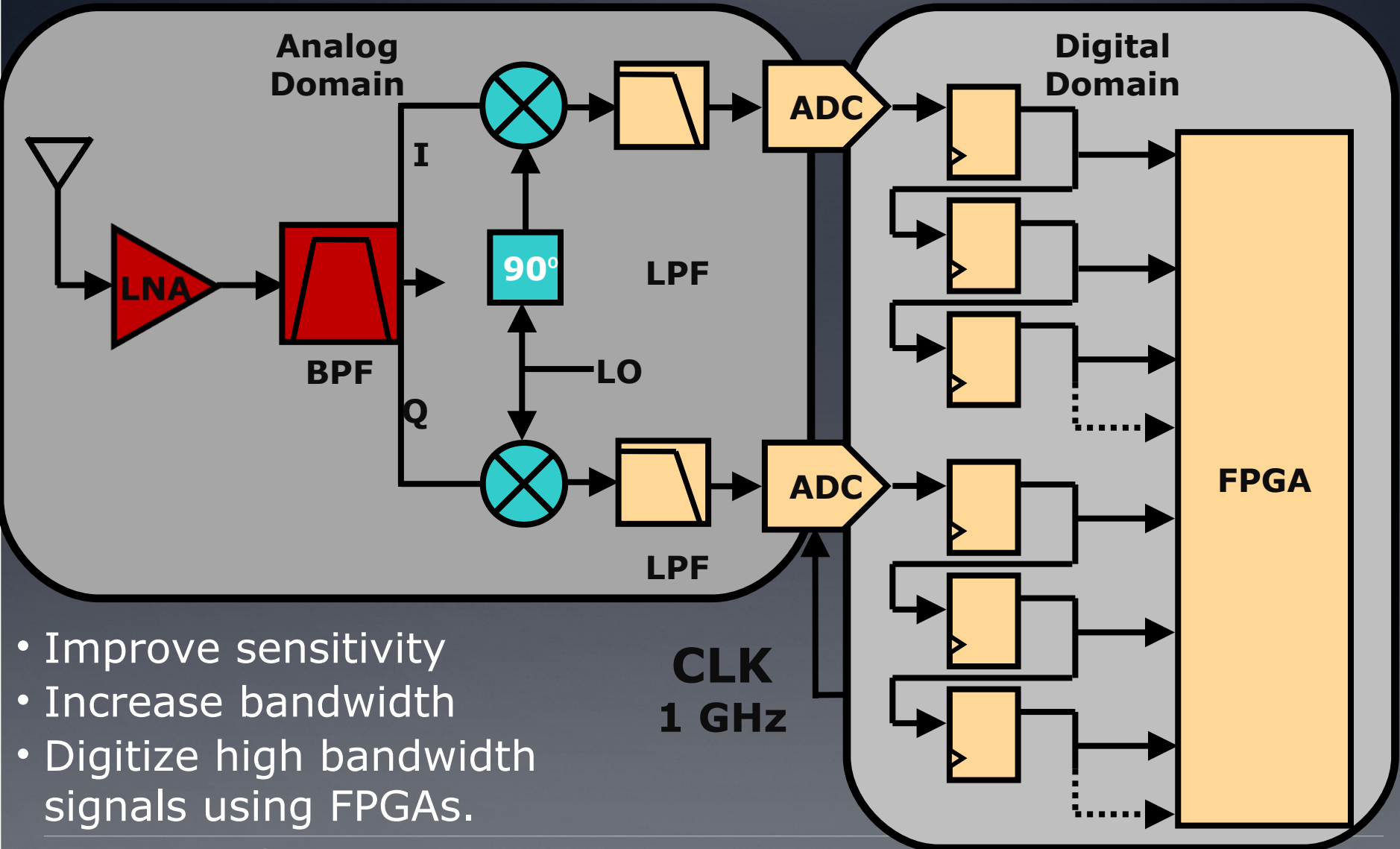


- Improve sensitivity
- Increase bandwidth
- Digitize high bandwidth signals using FPGAs.

Future

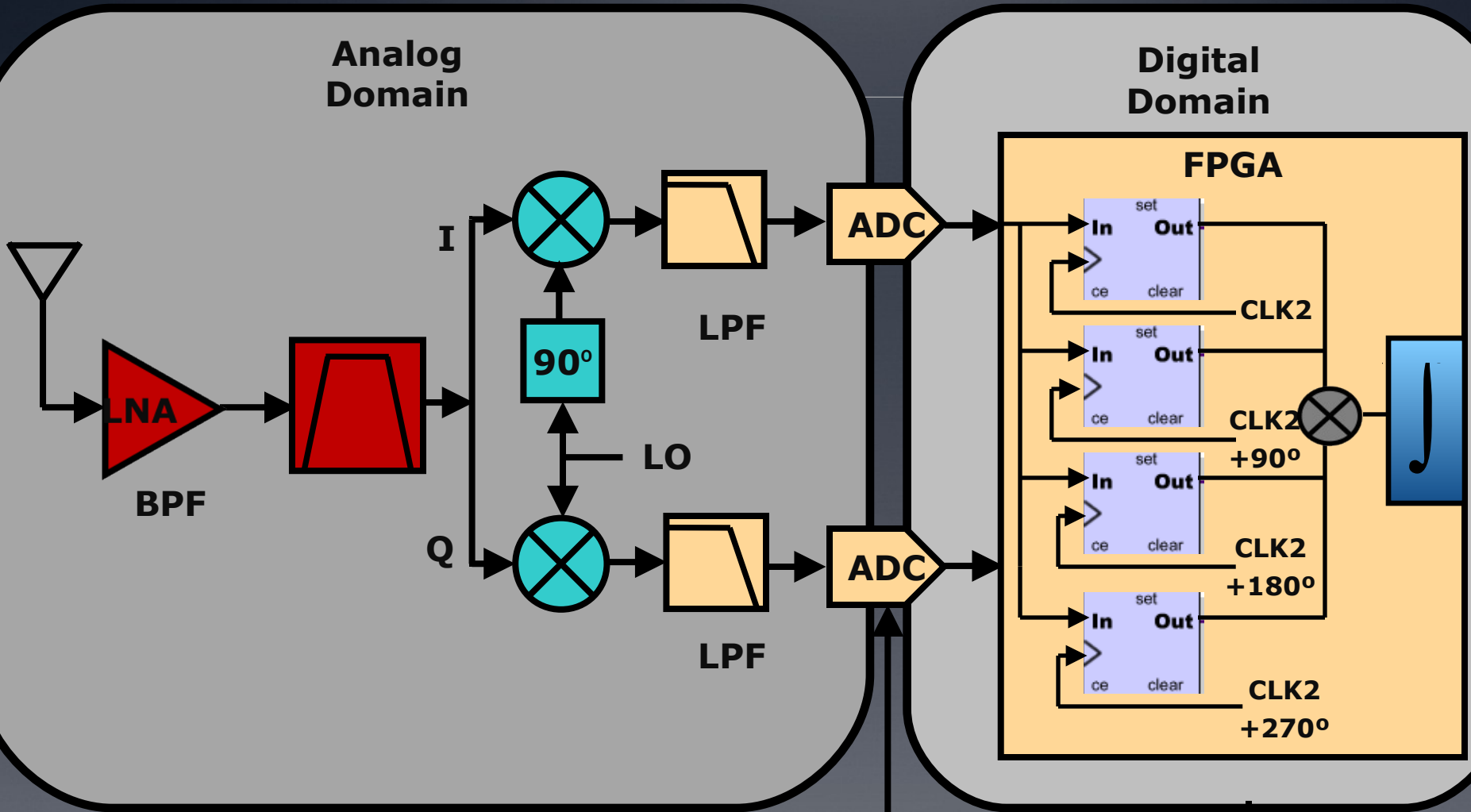

Suitable to SKA correlators

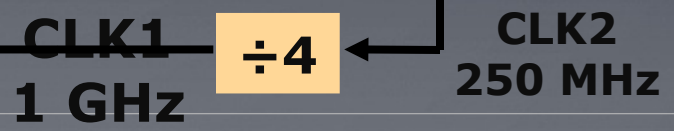

FIM

Muchas Gracias